

**FACULTY OF ENGINEERING & TECHNOLOGY,
UNIVERSITY OF LUCKNOW
B.TECH. SEMESTER - IV, 2023-24
Branches: ECE, CSE & AI**

Student's Roll No.....

Subject Code: EC-301

Subject Title: Digital Circuits & Logic Design

Time: 1 Hrs.

Full Marks: 20

Note: Attempt questions from each section as per instructions.

SECTION A

1. Attempt all parts of this question. Each part carries 1 mark. (1 x 5=5)

- a) What are universal logic gates? Why they are called as universal logic gates?
- b) Explain in brief ASCII code.
- c) Implement XNOR gate using NAND gate.
- d) Convert $(BF.34)_{16}$ into equivalent binary and octal code.
- e) Convert $(35.35)_{10}$ into equivalent hexadecimal code.

SECTION B

Attempt any THREE questions of the following. Each question carries equal marks. (5 x 3=15)

2. Simplify the given expression using Boolean theorems:

$$F(A, B, C) = \bar{A}BC + B\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}B + A\bar{C} + ABC.$$

3. Generate the Hamming code for the message bit 111011. Also check whether received code word 1110010011 is erroneous or not. If yes, then find out that position. *(even parity)*

4. Find out the minterms and maxterms of given expression:

$$F(A, B, C, D) = AB + CD.$$

OR

Perform subtraction (A-B) between A=1011 and B=1110 using 2's complement method and BCD addition (A+B) between A=6 and B=8.

5. Explain and classify binary codes in detail with suitable examples.

OR

Simplify the following Boolean function using K-map and also implement the simplified function using logic gates:

$$F(A, B, C, D) = \sum m(0, 2, 4, 5, 7, 10, 11, 13, 14, 15) + \sum d(1, 8, 12).$$

**Department of Electronics and Communication Engineering,
Faculty of Engineering & Technology, University of Lucknow
2nd Mid Term Exam (2023-24)**

Digital Circuits and Logic Design (EC-301)

M.M.: 20

Time: 1 HOUR

NOTE: Attempt all the questions.

Roll. No.....

SECTION-A

1. Note: Attempt all the parts. (1x5=5)

- ☒ a) Differentiate combinational and sequential circuits.
- ☒ b) Design XOR and XNOR gate using 2:1 MUX.
- ☒ c) Define race-around condition only.
- ☒ d) Give the excitation tables for S-R and J-K flipflops.
- e) Calculate total time required in load and shift by a 4-bit SISO shift register if each flip-flop has 10 ns propagation delay.

SECTION-B

Note: Attempt any three questions. (5x3=15)

- ☒ 2. Design a 4-bit magnitude comparator with its output expressions.
- ☒ 3. Design a 16:1 MUX using 4:1 MUX only. Also, implement the given function using 4:1 MUX taking A&B as select lines:
$$F(A,B,C,D) = \sum m(0,1,2,4,5,8,10,12,14).$$
- 4. Draw and explain PISO shift right register with its timing diagram.
- 5. Draw and explain ring and Johnson counters with their timing diagrams.

8325

B.Tech. IIIrd Semester Examination, 2023

**DIGITAL CIRCUITS AND LOGIC
DESIGN**

Paper : EC-301

Time : 3 Hours]

[M.M. : 70

Note :- Answer any *five* questions. All questions carry equal marks.

✓ 1. (a) ✓ What do you understand by weighted and non-weighted binary codes ? Convert Gray code 1101 to equivalent excess-3 code.

✓ (b) ✓ What are universal logic gates ? Why are they called as universal logic gates ? Design XNOR gate and AND gate using NOR gates.

✓ 2. (a) ✓ Find out the minterms and maxterms for the given function :

$$F(A, B, C, D) = AB + CD$$

- (b) Simplify the following Boolean function 'F' together with don't-care condition and also implement the simplified function using NAND gate only :

$$F(A, B, C, D) = \Sigma m(1, 3, 5, 7, 9) +$$

$$d(A, B, C, D) = \Sigma m(6, 12, 13)$$

3. (a) Simplify the following function using tabulation method :

$$F(A, B, C, D) = \Sigma m(1, 4, 6, 7, 8,$$

$$9, 10, 11, 15)$$

- (b) Perform the subtraction $(A - B)$ using 1's complement method where $A = 1011$ and $B = 1110$. Also, draw its circuit diagram.

4. (a) Write the BCD equivalent of $(AB)_{16}$. Perform BCD addition between $A = 7$ and $B = 9$ with its circuit diagram.

- (b) Design a 16 : 1 multiplexer using 4 : 1 multiplexer. Also, implement the following Boolean function using 4 : 1 MUX taking C and D as select line :

$$F(A, B, C, D) = \Sigma m(0, 1, 2, 3, 4, 6,$$

$$8, 10, 12, 13, 14, 15)$$

5. (a) Draw and explain a 4-bit magnitude comparator with its output expressions.

- (b) Differentiate between characteristic table and excitation table. Explain race-around condition in detail with its remedies.

6. (a) Perform the following conversions :

(i) J-K flipflop to T flipflop

(ii) D flipflop to J-K flipflop

- (b) Explain 4-bit ring counter and Johnson counter using D-flipflop with its timing diagrams.


7. (a) Design 4-bit synchronous counter using D flipflop and also trace its timing diagram.

- (b) Design Modulo-14 synchronous counter using S-R flipflops.


8. (a) Draw and explain 4-bit PISO shift-left register using D-flipflop.

- (b) Differentiate between synchronous and asynchronous sequential circuits. Calculate total time required in load and shift by 4-bit PISO shift register if each flipflop has 15 ns propagation delay.

 9. (a) Derive state table and state graph for the following circuit diagram :



 - (b) Draw the reduced state graph by first deriving its reduced state table of the following state graph :



10. (a) Discuss the characteristic parameters of a logic family. Calculate the fan-out of an inverter having the following specifications :

$$I_{OH \max} = -0.4\text{mA}, I_{OL \max} = 8\text{mA}, I_{IH \max} = 20\mu\text{A}, I_{IL \max} = -0.1\text{mA}.$$

- (b) Implement the following function using PROM, PLA and PAL :

$$F(A, B, C, D) = \sum m(0, 3, 6, 9, 10, 12, 14, 15)$$